



1.2 If the things we need to do in a processor are fetch consecutive instructions (Figure 4.6) and decode the instruction, what would the cycle time be?

PC I-MEM

$$0 + 200ps = 200ps$$

A: 200 ps

 


FIGURE 4.6 A portion of the datapath used for fetching instructions and incrementing the program counter. The fetched instruction is used by other parts of the datapath.

1.3. If this processor only needs to support **sw** and **beq** and **sub** instructions, what is the clock cycle time? (Hint: You should analyze the critical path of the required instructions)

$$sw: \frac{200}{I-MEM} + \frac{200}{Control} + \frac{60}{ALU\ Control} + \frac{120}{ALU} + \frac{200}{Data\ MEM} = 780ps \#$$

$$beq: \frac{200}{I-MEM} + \frac{200}{Control} + \frac{60}{ALU\ Control} + \frac{120}{ALU} + \frac{50}{AND} + \frac{40}{MUX} = 670ps$$

$$sub: \frac{200}{I-MEM} + \frac{200}{Control} + \frac{60}{ALU\ Control} + \frac{120}{ALU} + \frac{40}{MUX} = 620ps$$

ANS: 780 ps #

1.4. What is the clock cycle time of this processor that supports the instructions listed in Table 2? (Hint: lw 請使用 I-Mem + Ctrl Unit + ALU Ctrl + ALU + Data-Mem + Mux 公式計算)

$$lw: \frac{200}{I-MEM} + \frac{200}{Control} + \frac{60}{ALU\ Control} + \frac{120}{ALU} + \frac{200}{Data\ Mem} + \frac{40}{MUX} = 820ps$$

$$add: \frac{200}{I-MEM} + \frac{200}{Control} + \frac{60}{ALU\ Control} + \frac{120}{ALU} + \frac{40}{MUX} = 620ps$$

ANS: 820ps #

2. In this exercise we examine in detail how an instruction is executed in a single-cycle datapath. Problems in this exercise refer to **3 clock** cycle in which the processor fetches the following **3 instructions word**:

$\begin{matrix} \text{op} & \text{rs (9)} & \text{rt (6)} & \text{rd (11)} & \text{shamt} & \text{func} \\ \hline 0000 & 0001 & 0010 & 1010 & 0101 & 1000 & 0010 & 0010 \end{matrix}$   
**sw \$8, 2(\$9)**  
**beq \$8, \$(9), 20**

Assume that **data memory is all zeros** and that the **processor's registers have the following values** at the beginning of the cycle in which the above instruction word is fetched (Please refer to the MIPS Instruction Opcode & Funct fields listed in *Table 2*):

| <i>r0</i> | <i>r1</i> | <i>r2</i> | <i>r3</i> | <i>r4</i> | <i>r5</i> | <i>r6</i> | <i>r8</i> | <i>r9</i> | <i>r10</i> | <i>r11</i> | <i>r31</i> |
|-----------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|------------|------------|------------|
| 0         | -1        | 9         | -3        | -4        | 10        | 11        | 8         | 5         | 7          | 4          | -16        |

 


Figure 2.

- 2.1. What are the **3** outputs of the sign-extend and the jump "Shift left-2" unit (near the top of Figure 4.24) for this instruction word?

Instruction 1 : **sub \$11, \$9, \$10** (000000 01001 01010 01011 00000 100010)  
 Sign Extended = 00000000 00000000 01011000 00100010 #  
 Shift Left -2 = 0100 10101001 01100000 10001000 #  
 2 : **sw \$8, 2(\$9)** (101011 01001 01000 00000000 00000010)  
 Sign Extended = 00000000 00000000 00000000 00000010 #  
 Shift Left -2 = 01001 01000 00000000 0000001000 #  
 3 : **beq \$8, \$9, 20** (000100 01000 01001 00000000 00010100)  
 Sign Extended = 00000000 00000000 00000000 00010100 #  
 Shift Left -2 = 01000 01001 00000000 0001010000 #

2.2. What are the values of the ALU control unit's inputs for **these instructions**?

| Instruction | RegDst | ALUSrc | Memto-Reg | Reg Write | Mem Read | Mem Write | Branch | ALUOp1 | ALUOp0 |
|-------------|--------|--------|-----------|-----------|----------|-----------|--------|--------|--------|
| R-format ✓  | 1      | 0      | 0         | 1         | 0        | 0         | 0      | 1      | 0      |
| lw          | 0      | 1      | 1         | 1         | 1        | 0         | 0      | 0      | 0      |
| sw ✓        | X      | 1      | X         | 0         | 0        | 1         | 0      | 0      | 0      |
| beq ✓       | X      | 0      | X         | 0         | 0        | 0         | 1      | 0      | 1      |

| Instruction | ALU <sub>OP(1)</sub> | ALU <sub>OP(0)</sub> | Instructions (6bit) |
|-------------|----------------------|----------------------|---------------------|
| 1           | 1                    | 0                    | 100010              |
| 2           | 0                    | 0                    | 000010              |
| 3           | 0                    | 1                    | 010100              |

2.3. What is the new PC address after **these instructions are** executed? **And, highlight** the path through which this value is determined.

Ans: (1)  $PC_{new} = PC_{old} + 4$

(2) 答案已標示在 Figure 2

2.4. For each Mux, show **the control signal of Mux and** the values of its data output during the execution of **these instructions and these register values**.

| RegDst Mux |    | ALUSrc Mux |   | PCsrc Mux |      | MemtoReg Mux |    |
|------------|----|------------|---|-----------|------|--------------|----|
| 1          | 11 | 0          | 7 | 0         | PC+4 | 0            | -2 |
| X          | X  | 1          | 2 | 0         | PC+4 | X            | X  |
| X          | X  | 0          | 5 | 0         | PC+4 | X            | X  |

2.5. For the ALU and the two add units, what are their data input values?

| ALU  | Add   | Add (ALU result) |          |          |                       |
|------|-------|------------------|----------|----------|-----------------------|
| 5, 7 | PC, 4 | PC+4,            | 00000000 | 00000001 | 01100000 10001000 (2) |
| 5, 2 | PC, 4 | PC+4,            | 00000000 | 00000000 | 00000000 00001000 (2) |
| 8, 5 | PC, 4 | PC+4,            | 00000000 | 00000000 | 00000000 01010000 (2) |

2.6. What are the values of all inputs for the "Registers" unit?

| Read Register 1 | Read Register 2 | Write Register | Write Data | RegWrite |
|-----------------|-----------------|----------------|------------|----------|
| 9               | 10              | 11             | -2         | 1        |
| 9               | 8               | X              | X          | 0        |
| 8               | 9               | X              | X          | 0        |

3. Given a processor implemented by a single-cycle control and datapath shown in follow. Assume that the functional blocks adopted to implement the datapath have the following latencies:

 


Figure 3.

| Inst.-Mem. | Add   | Mux   | ALU   | ALU-Ctrl | Regs. Access | Data-Mem. | Sign-extend | Shift-left-2 |
|------------|-------|-------|-------|----------|--------------|-----------|-------------|--------------|
| 500ps      | 350ps | 100ps | 250ps | 100ps    | 400ps        | 600ps     | 100ps       | 50ps         |


- 3.1. For add instruction's critical path shown in Figure, **which control signal is the most critical** that is needed to be quickly generated, and **what is the maximum time** that the control unit can generate this signal to avoid lengthening the critical path? (Hint: the critical path of add instruction)

$$\text{ALU Source MUX Input delay} = \frac{500}{\text{INS-MEM}} + \frac{400}{\text{REG-FILE}} = 900$$

Control Input delay =  $\frac{500}{\text{INS-MEM}}$

$$900 - 500 = 400$$

A: (1) ALU Src MUX (2) 400ps

 

3.2. Assume that the control unit shown in Figure requires the times to generate the individual control signals as the following table. What is the clock cycle time of this processor?

| RegDst | Jump   | Branch | MemRead | MemtoReg | ALUOp | MemWrite | ALUSrc | RegWrite |
|--------|--------|--------|---------|----------|-------|----------|--------|----------|
| 1440ps | 1000ps | 1000ps | 600ps   | 1000ps   | 500ps | 800ps    | 350ps  | 1300ps   |

$$I_w : 500_{(I-MEM)} + 500_{(ALU-OP)} + 100_{(ALU-Ctrl)} + 250_{(ALU)} + 600_{(Data-MEM)} + 100_{(MUX)} = 2050$$

$$SW : 500_{(I-MEM)} + 500_{(ALU-OP)} + 100_{(ALU-Ctrl)} + 250_{(ALU)} + 600_{(Data-MEM)} = 1950$$

$$R-Format : 500_{(I-MEM)} + 1440_{(Reg-Dst)} + 100_{(MUX)} = 2040$$

$$A : 2050 \text{ ps}$$

3.3 If the only thing we need to do in a processor is fetch consecutive instructions (Figure 4.6), what would the cycle time be?

$$500_{(I-MEM)}$$

$$A : 500 \text{ ps}$$

3.4 Consider a datapath similar to the one in Figure 4.11, but for a processor that only has one type of instruction: unconditional PC-relative branch. What would the cycle time be for this datapath?

$$500_{(I-MEM)} + 100_{(Sign-Ext)} + 50_{(Shift-2)} + 350_{(ADD)} + 100_{(MUX)} = 1100 \quad A : 1100 \text{ ps}$$

3.5 Repeat 3.4, but this time we need to support only conditional PC-relative branches.

$$500_{(I-MEM)} + 1000_{(Branch)} + 100_{(MUX)} = 1600$$


$$A : 1600 \text{ ps}$$

3.6 Which kinds of instructions require the datapath element Shift-left-2 resource? For which kinds of instructions (if any) is this resource on the critical path?

Ans: (1) beq, j 指令

(2) 在 beq 中不是 critical path, 因為 Control Branch 的時間遠大於 Sign-ext + Shift-2-left。在 j 指令中即是 critical path, ADD 遠小於 Sign-ext + Shift-2-left。

4. When processor designers consider a possible improvement to the processor data path, the decision usually depends on the cost/performance trade-off. In the following three problems, assume that we are starting with a data path from Figure 4.2, where I-Mem, Add, Mux, ALU, Registers, D-Mem, and Control blocks have latencies of 500ps, 200ps, 50ps, 200ps, 300ps, 450ps, and 100ps, respectively, and costs of 1500, 35, 20, 100, 200, 2000, and 500 (dollars), respectively. Consider the addition of a multiplier to the ALU. This addition will add 350ps to the latency of the ALU and will add a cost of 580 dollars to the ALU. The result will be 10% fewer instructions executed since we will no longer need to emulate the MUL instruction.

 

**FIGURE 4.2** The basic implementation of the MIPS subset, including the necessary multiplexors and control lines. The top multiplexor ("Mux") controls what value replaces the PC (PC + 4 or the branch destination address); the multiplexor is controlled by the gate that "ANDs" together the Zero output of the ALU and a control signal that indicates that the instruction is a branch. The middle multiplexor, whose output returns to the register file, is used to steer the output of the ALU (in the case of an arithmetic-logical instruction) or the output of the data memory (in the case of a load) for writing into the register file. Finally, the bottommost multiplexor is used to determine whether the second ALU input is from the registers (for an arithmetic-logical instruction or a branch) or from the offset field of the instruction (for a load or store). The added control lines are straightforward and determine the operation performed at the ALU, whether the data memory should read or write, and whether the registers should perform a write operation. The control lines are shown in color to make them easier to see.

|         | I-Mem | Add   | Mux  | ALU   | ALU With Multiplier | Regs  | D-Mem | Control |
|---------|-------|-------|------|-------|---------------------|-------|-------|---------|
| latency | 500ps | 200ps | 50ps | 200ps | 550ps               | 300ps | 450ps | 100ps   |
| cost    | 1500  | 35    | 20   | 100   | 680                 | 200   | 2000  | 500     |

4.1 What is the clock cycle time with and without this improvement?

$$\text{Without: } \frac{500}{\text{I-MEM}} + \frac{300}{\text{Regs}} + \frac{50}{\text{MUX}} + \frac{200}{\text{ALU}} + \frac{50}{\text{MUX}} + \frac{450}{\text{D-MEM}} = 1550$$

$$\text{With: } \frac{500}{\text{I-MEM}} + \frac{300}{\text{Regs}} + \frac{50}{\text{MUX}} + \frac{350+200}{\text{ALU-Latency}} + \frac{50}{\text{MUX}} + \frac{450}{\text{D-MEM}} = 1900 \quad (1) \text{ Without: } 1550 \text{ ps}$$

A: (2) With: 1900 ps

4.2 What is the speedup achieved by adding this improvement?

$$\frac{1}{0.9} \times \frac{1550}{1900} \approx 0.9064$$

$$A: 0.906$$



4.3 Compare the cost/performance ratio with and without this improvement.

$$Cost_{old} = \frac{1500}{I-MEM} + \frac{35 \times 2}{Add} + \frac{20 \times 3}{MUX} + \frac{100}{ALU} + \frac{200}{Regs} + \frac{2000}{D-MEM} + \frac{500}{Control} = 4430 \text{ ps}$$

$$Cost_{new} = \frac{1500}{I-MEM} + \frac{35 \times 2}{Add} + \frac{20 \times 3}{MUX} + \frac{680}{ALU} + \frac{200}{Regs} + \frac{2000}{D-MEM} + \frac{500}{Control} = 5010 \text{ ps}$$

$$CP = \frac{5010}{4430} \times \frac{1900}{1550} \times 0.9 \cong 1.247$$

$$A: 1.25$$

5. Assume that there are no pipeline stalls and that the breakdown of executed instructions is as follows

| add | addi | not | beq | lw  | sw  |
|-----|------|-----|-----|-----|-----|
| 25% | 15%  | 0%  | 25% | 20% | 15% |

5.1 In what fraction of all cycles is the data memory used?

$$\frac{20\%}{lw} + \frac{15\%}{sw} = 35\%$$

ANS: 35%

5.2 In what fraction of all cycles is the input of the sign-extend circuit needed? What is this circuit doing in cycles in which its input is not needed?

$$\frac{15\%}{addi} + \frac{25\%}{beq} + \frac{20\%}{lw} + \frac{15\%}{sw} = 75\%$$

ANS: 75%

5.3 In what fraction of all cycles is the "MemtoReg Mux" used?

$$\frac{25\%}{add} + \frac{15\%}{addi} + \frac{20\%}{lw} = 60\%$$

ANS: 60%

5.4 In what fraction of all cycles is the "ALUSrc Mux" used?

$$\frac{25\%}{add} + \frac{15\%}{addi} + \frac{25\%}{beq} + \frac{20\%}{lw} + \frac{15\%}{sw} = 100\%$$

ANS: 100%